



DEPARTMENT OF PHYSICS
MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR

MONOSTABLE MULTIVIBRATOR


Aim: To set up and study a monostable multivibrator using transistors.

Components and equipments required Transistors, resistors, capacitors, signal generator, dc power source, bread board and CRO.

Theory This multivibrator has only one stable state as its name suggests. It has one quasi-stable state also. An external trigger forces this circuit to go to quasi-stable state from its stable state and remain in that state for an amount of time determined by the discharging time of the capacitor. R and C are the timing elements and C₁ is the speed up capacitor.

Figure shows a monostable multivibrator using single bias supply. As soon as the power supply is switched ON, transistor Q₁ goes to cut off state and Q₂ goes to saturation state due to regenerative action. The stable state voltages are V_{c1} = V_{cc}, V_{c2} = V_{CE}(sat), V_{B1} = -V_f, and V_{B2} = V_{BE}(sat). The moment a negative trigger is applied at the collector of the transistor Q₁, transistor Q₂ goes to cut off state. Hence V_{c2} jumps to V_{cc}. This sudden change is coupled to the base of the transistor Q₁ and hence it goes to ON state. The collector voltage of the transistor Q₁ suddenly drops by an amount I_{c1}R_{c1}, where I_{c1} is the current through the resistance R_{c1}. Since capacitor acts as a short circuit for a sudden change, the base voltage of Q₂ suddenly drops by an equal amount. Now the polarity of the charge of the capacitor is such a way that the negative is at its right side. Now capacitor charges from this negative potential to +V_{cc} through R and Q₁. Capacitor discharges through the ON transistor. Once it becomes zero it further charges towards V_{cc}. But, when the positive potential at the right side of the capacitor reaches the cut in voltage, Q₂ turns ON. Thus the circuit comes back to the stable state. It will continue till the next trigger comes at the base of Q₂. The time duration of the quasi-stable state is given by the expression $T = 0.69 RC$.

Circuit diagram

 



DEPARTMENT OF PHYSICS
MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR

Design Output requirements Amplitude = 10 V, pulse width = 1ms.

Selection of transistor and diode Choose transistors BC 107 and diode 1N4001.

DC bias conditions $V_{CC} = 10 \text{ V}$, $V_{RE} = 2 \text{ V}$

Design of R_E $R_E = V_{RE} / I_E = 1 \text{ k}$ Since $I_E = I_C$

Design of R_1 and R_2 Consider the astable state (Q_1 is OFF and Q_2 is ON)

Assume $V_{BE} = -1 \text{ V}$ to assure that the transistor is in cut off state. Then $V_{B1} = 2 - (-1) = 1 \text{ V}$.

Since $I_{B1} = 0$, current flowing through $R_2 =$ current flowing through R_1

$$V_{B1} = \frac{V_{C2} R_1}{R_1 + R_2} = \frac{2.3 \text{ V} \times R_1}{R_1 + R_2}$$

From this, $R_2 = 1.3 R_1$

Consider the astable state (Q_1 is ON and Q_2 OFF):

$V_{C2} = 12 \text{ V}$ since Q_2 is OFF.

$V_{B1} = V_{BEsat} + V_{RE} = 2.8 \text{ V}$

Also, $I_{R2} = I_{B1} + I_{R1}$

$$\text{i.e., } \frac{12 \text{ V} - 2.8 \text{ V}}{R_2} = I_{B1} + \frac{2.8 \text{ V}}{R_1}$$

Substituting the value of R_2 we get $9.2 R_1 = 1.3 \times 10^{-4} \times R_1^2 + 3.64 \times R_1$
 or $1.3 \times 10^{-4} \times R_1^2 - 5.56 \times R_1 = 0$

Solving this quadratic expression

$$R_1 = + \frac{-5.56 \pm \sqrt{31}}{2 \times 1.3 \times 10^{-4} \times R_1^2} = 42.8 \text{ k. Use } 47 \text{ k std.}$$

Then $R_2 = 55.64 \text{ k}$ use 56 k std.

Design of R_{C1} and R_{C2} $R_C = \frac{V_{CC} - V_C}{I_{Csat}} = 4.35 \text{ k. Use } 4.7 \text{ k std.}$

Take $R_{C1} = R_{C2} = R_C$

Design of R R must be able to provide base current enough to keep the transistors in saturation.

$$I_B \text{ min} = I_C / h_{FE} = 2 \text{ mA} / h_{FE} = 20 \mu\text{A}$$

Consider an over-driving factor 5, so that transistor will be indeed in saturation.

Then actual base current $I_B = 5 I_B \text{ min} = 0.1 \text{ mA}$

$$R = (V_{CC} - V_{BE \text{ sat}}) / 0.1 \text{ mA} = 73 \text{ k. Use } 82 \text{ k.}$$

We have $T = 0.69RC$. substituting the value of R we get, $C = 0.01 \mu\text{F}$.

Design of differentiator circuit: The condition is $R_d C_d < 0.0016T_t$, where $T_t =$ time period of trigger signal. To avoid the loading of the signal generator by the differentiator, take $R_d = 6.8 \text{ k}$.

Let T_t be 2 ms . Then $C_d = 0.01 \mu\text{F}$.




DEPARTMENT OF PHYSICS
MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR

Procedure

1. Test all components and probes before rigging up the circuit.
2. Switch ON V_{CC} supply and verify Q_1 is in OFF state and Q_2 is in ON state. V_{C1} should be high and V_{C2} should be low.
3. Switch ON trigger supply. Trigger should have sufficient amplitude.
4. Observe the collector and base waveforms of both transistors. Note down all aspects of the waveforms such as the pulse width, amplitudes, overshoots etc.

Waveforms

 

Reference

Electronics Lab Manual Volume I, K.A. Navas, **Rajath Publishers**