



DEPARTMENT OF PHYSICS  
MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR

**UJT CHARACTERISTICS**

**Aim** To plot the VI characteristics of a unijunction transistor and to measure its intrinsic stand off ratio.

**Components and equipments required** UJT, voltmeters, ammeters, rheostats, dc sources, bread board and CRO.

**Theory** A unijunction transistor consists of a bar of highly doped N-type semiconductor to which a heavily doped P-type rod is attached. Ohmic contacts are made at opposite ends of the N-type bar, which are called base<sub>1</sub>(B<sub>1</sub>) and base<sub>2</sub>(B<sub>2</sub>) of the transistor. P-type rod is called the emitter.

Refer the equivalent circuit of the UJT given in figure. The inter base resistance  $R_{BB}$  of the N-type silicon bar appears as two resistors  $R_{B1}$  and  $R_{B2}$ , where  $R_{BB}$  equals the sum of  $R_{B1}$  and  $R_{B2}$ . The intrinsic stand off ratio  $\eta$  is given by the expression

$$\eta = \frac{R_{B1}}{R_{BB}} \text{ with } I_E = 0$$

Due to the applied voltage at the B<sub>2</sub> of the transistor, a positive voltage gets developed across  $R_{B1}$  and is equal to  $\eta V_{BB}$ .

When  $V_E$  is less than the voltage across  $R_{B1}$ , diode becomes reverse biased. When  $V_E$  increases, a forward current flows through the emitter to B<sub>1</sub> region.

If  $V_E$  is raised further, a sudden reduction of  $R_{B1}$  occurs. This happens because the increase in current reduces  $R_{B1}$ . Reduction in  $R_{B1}$  causes the increase in current through it. This further reduces  $R_{B1}$  and so forth. In other words, a regenerative action takes place at a particular value of  $V_E$ , called peak voltage which is expressed as  $V_P = \eta V_{BB} + V_D$ , where  $V_{BB}$  is the base supply voltage and  $V_D$  is the junction voltage drop. After a particular value of  $V_E$ , called valley point, emitter current increases with  $V_E$ , similar to that of an ordinary forward biased diode.

As explained above, when  $V_E$  is rises, forward resistance across the junction decreases and the junction behaves as a short circuit. Then current through the E-B<sub>1</sub> junction increases and hence voltage across the junction decreases. This is equivalent to a negative resistance



**DEPARTMENT OF PHYSICS**  
**MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR**



across the junction. This continues up to a voltage called valley voltage  $V_V$  after which junction behaves as an ordinary diode.

**Procedure**


1. Identify the leads of UJT correctly and set up the circuit as shown in figure.
2. Keeping  $V_{BB} = 0$ , Vary  $V_E$  from 0 V to 10 V in steps of 0.5 V. Take the voltmeter and ammeter readings at the input side and enter it in tabular column. Repeat it for other values of  $V_{BB}$  (say 3 V & 6 V).
3. Plot the VI characteristics with  $I_E$  along x-axis and  $V_E$  along y-axis.
4. Calculate the intrinsic stand off ratio from the graph using its expression.

Note: Since peak current  $I_p$  is in  $\mu A$ , initial rise of voltage in the graph may not be obtained.

**Circuit diagram**

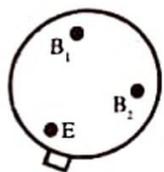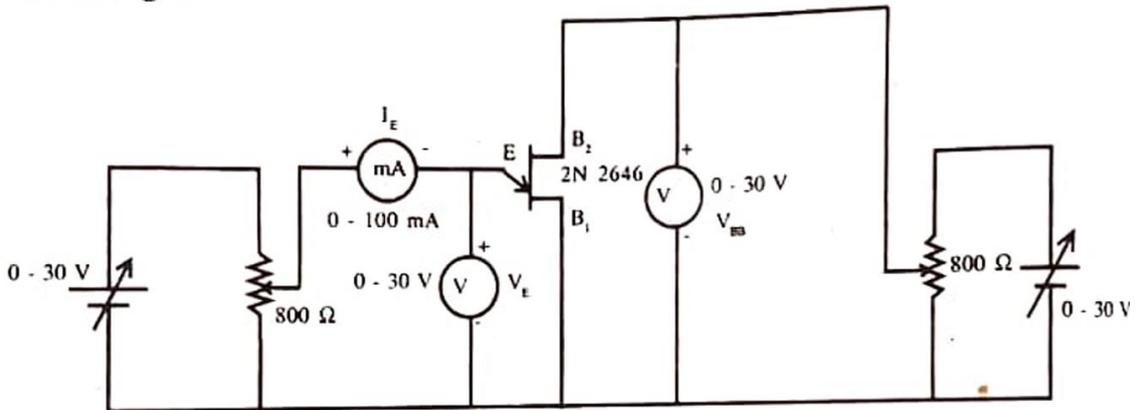

Pin out of 2N 2646

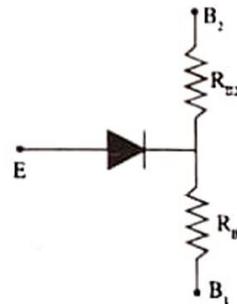

Equivalent circuit of UJT

**Details of 2N 2646**  $\eta_{min} = 0.56$ ,  $\eta_{max} = 0.75$   
 $I_p \text{ max} = 5 \mu A$  and  $I_V \text{ min} = 4 \text{ mA}$


**Tabular column**

$V_{BB} = 0 \text{ V}$		$V_{BB} = 3 \text{ V}$		$V_{BB} = 6 \text{ V}$	
$V_E \text{ V}$	$I_E \text{ mA}$	$V_E \text{ V}$	$I_E \text{ mA}$	$V_E \text{ V}$	$I_E \text{ mA}$



DEPARTMENT OF PHYSICS  
MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR

Graph

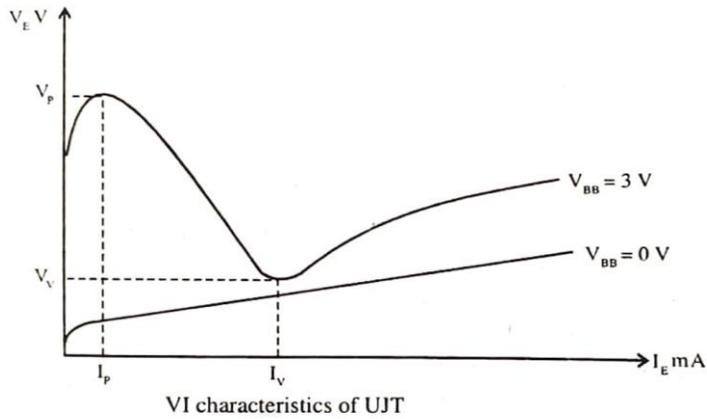

$$\eta = \frac{V_P - V_D}{V_{BB}} = \dots\dots\dots$$

Result Intrinsic stand off ratio  $\eta = \dots\dots\dots$

**Reference**

Electronics Lab Manual Volume I, K.A. Navas, **Rajath Publishers**