



DEPARTMENT OF PHYSICS  
MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR

**RC HIGH PASS FILTER**

**Aim** To design and set up a high-pass RC filter for a 3-dB frequency of 1 kHz and study its frequency response.

**Components and equipments required** Capacitor, resistor, signal generator, bread board and CRO.

**Theory** An high pass filter can be made from the low pass filter by merely interchanging its resistance and capacitor. Since the reactance of the capacitor decreases with increase in frequency, the higher frequency components in the input signal appear at the output with less attenuation than the lower frequency components. In other words, lower frequencies are attenuated by the circuit. At high frequencies, the capacitor acts almost as a short circuit and virtually the input amplitude appears at the output. Hence, this kind of circuit is called a high pass filter.


The magnitude of the ratio of output voltage to input voltage of the circuit is given by

$$A = \frac{1}{\sqrt{1 + (f_L/f)^2}} \quad \text{where } f_L = \frac{1}{2\pi RC} \text{ and } f = \text{input signal frequency.}$$

$$\text{When } f = f_L, A = 1/\sqrt{2} = 0.707.$$

It means that when input frequency becomes  $f_L$ , output becomes 70.7 % of its maximum level. 29.3% reduction in voltage corresponds to a gain reduction of 3 dB in dB scale.  $f_L$  is called half power frequency, resonant frequency or 3 dB frequency.

**Circuit diagram**

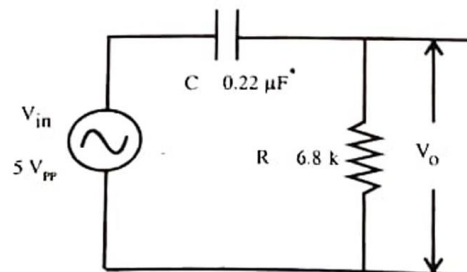

**Design** Let the lower cut off frequency  $f_L$  be 1 KHz.

$$\text{We have } f_L = 1/2\pi RC.$$

To avoid loading, as a thumb rule, select  $R =$  ten times the output impedance of the function generator. i.e.,  $R = 6000 \Omega$ . Use 6.8 k std.

Substituting this in the above expression we get,  $C = 0.023 \mu\text{F}$ . Use  $0.022 \mu\text{F}$ .




**DEPARTMENT OF PHYSICS**  
**MAR THOMA COLLEGE FOR WOMEN, PERUMBAVOOR**

**Procedure**

1. Set up the circuit after testing all components.
2. Observe the signal generator output (a sine wave with 5 V peak to peak) on one channel of the CRO.
3. Connect the input signal to the circuit and output to the other channel of CRO so that input and output can be observed simultaneously.
4. Vary the input frequency from 10 Hz to 100 kHz or more and note down the output voltage in tabular column.
5. Plot the graph on semilog graph sheet with frequency  $f$  (or  $\log f$ ) on x-axis and gain in dB on y-axis.
6. Mark a point on the graph at 3-dB less than the maximum gain. Extend the point to x-axis and mark the lower 3-dB frequency.

**Tabulation**

$V_{in} = 5 V_{pp}$		
$f$ in Hz	$V_O$ in volts	$A_V$ in dB

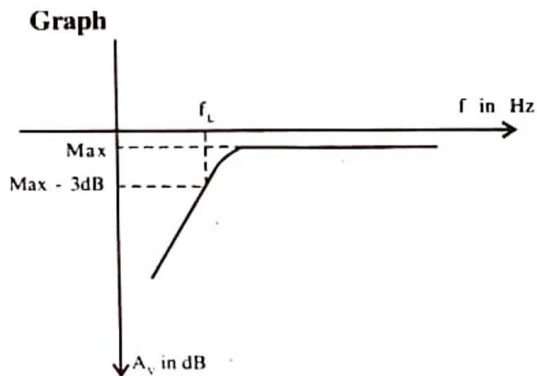

**Result** Theoretical 3-dB frequency = .....Hz  
Observed 3-dB frequency = .....Hz

**Reference**

Electronics Lab Manual Volume I, K.A. Navas, **Rajath Publishers**