

VERIFICATION OF DE MORGAN'S THEOREMS USING IC 7400

De Morgan's theorems are fundamental principles in Boolean algebra that describe the relationship between logical operations. These theorems state that the complement of a logical operation is equivalent to the logical operation performed on the complements of its inputs

Aim

To verify Dr Morgan's theorems using IC 7400



<u>To Prove Law I.</u> $\overline{A + B} = \overline{A} \cdot \overline{B}$

NOR using NAND gates (L.H.S. of equation)





Output is obtained by connecting a voltmeter between pins 11 and 7 through a resistor $1k\Omega$. For R.H.S. of the equation



Inputs		-	5		
Α	В	A	в	A·B	
0	0	6V	6V	6V	
0	6V	6V	0	0	
6V	0	0	6V	0	
6V	6V	0	0	0	

SHALL MAN

Result

From the above two truth tables I law $\overline{A + B} = \overline{A} \cdot \overline{B}$ is proved.



Aim

<u>To Prove law II,</u> $\overline{A.B} = \overline{A} + \overline{B}$ L.H.S.

2	In	puts		
	Α	В	A·B	A · B
	0	0	0	6V
	0	6V	0	6V
	6V	0	0	6V
	6V	6V	6V	0

R.H.S.

Here two 7400 ICs are used



Truth	table	for	OR

Inputs		-	=	
Α	В	A	в	A+B
0	0	6V	6V	6V
0	6V	6V	0	6V
6V	0	0	6V	6V
6V	6V	0	0	0

In	Inputs				
Ā	B	Α	В	A·B	A·B
6V	6V	0	0	0	6V
6V	0	0	6V	0	6V
0	6V	6V	0	0	6V
0	0	6V	6V	6V	0
	In Ā 6V 6V 0 0 0	Inputs Ā B 6V 6V 6V 0 0 6V 0 0	Inputs Ā B A 6V 6V 0 6V 0 0 6V 0 0 0 6V 6V 0 6V 6V	Inputs Ā B A B 6V 6V 0 0 6V 0 0 6V 0 6V 6V 0 0 6V 6V 0 0 6V 6V 6V	$\begin{tabular}{ c c c c c c c } \hline Inputs & & & & \\ \hline \overline{A} & \overline{B} & A & B & A \cdot B \\ \hline $6V$ & $6V$ & 0 & 0 & 0 \\ \hline $6V$ & $6V$ & 0 & 0 & 0 \\ \hline 0 & $6V$ & $6V$ & 0 & 0 \\ \hline 0 & 0 & $6V$ & $6V$ & $6V$ \\ \hline \end{tabular}$



Result

From the truth tables II law, $\overline{A + B} = \overline{A \cdot B}$

References

- Experimental Physics II, For Fifth & Sixth Semester, BSc Degree Programme, Dr.P. Sethumadhavan, Prof. K.C. Abraham, Prof. Meppayil Narayanan, Prof. Philipson C Philip, Manjusha Publications
- https://youtu.be/6eecDBqaYFY?si=zLrQIRizRNx9fLNd

